

Transformer :-

- 1) Single phase transformer construction & Working, Emf equation & phasor diagram, Eq Ckt, testing of transformers, Efficiency & Regulation, parallel operation.
- 2) Transformer II :- (3-phase).
Open ckt & short ckt test, Efficiency Regulation, Autotransformer comparison with two winding transformer, on the basis of copper losses & volume of copper
(core loss test) (copper loss or load loss test).
- 3) Review of 3-phase & single phase ckt, magnetic ckt & Electromechanical energy conversion principle. Basis of static & rotating electrical machines, EMF equations.

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_1 I_1 = V_2 I_2$$

→ Transformer is a static which is used to increase or decrease voltage or current without changing its frequency.

$$E = -\frac{d\phi}{dt} \rightarrow E = 4.44 f \Phi_{max} N$$

* Derive the above formula?

$$E_1 = 4.44 f \Phi_{max} N_1$$

$$E_2 = 4.44 f \Phi_{max} N_2$$

$$\Rightarrow \boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2}}$$

Object power = Output power

$$V_1 I_1 = V_2 I_2$$

\Rightarrow

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

F-5 Bunder
Nagash Kothari
Jain Jain
Sankha Mehta.


On basis of construction to per voltage

as per power

as per phase

as per am.


core tube and
shell type

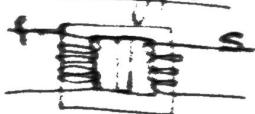

step up and
step down

when $E_2 > E_1$
 \downarrow
step up

when $E_1 > E_2$
 \downarrow
step down

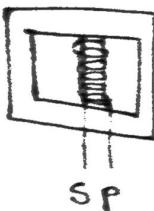

1) Distribution transformer single phase

2) Power transformer.

On our country generation
voltage is 11 KV

* 192 KV, 66 KV, 33 KV
used for distribution

→ Distribution transformer
is used for domestic
+ industrial purpose

directly
(11 KV/440, 11 KV/220)




→ One line +
One Neutral


3-phase

→ Three lines with
one neutral

(RYB) - With
Red Orange Blue One Black
Yellow Green Neutral

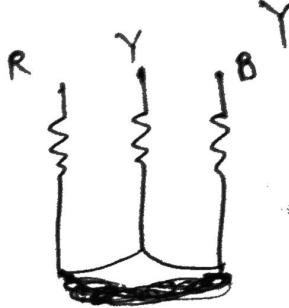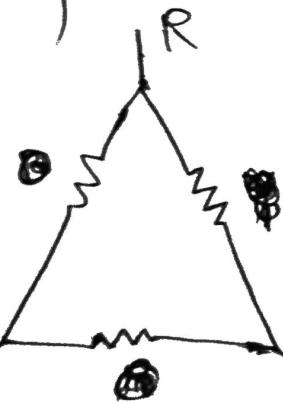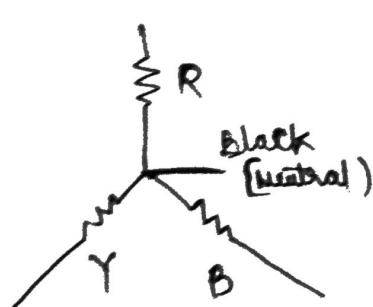Star-star
Star-delta
delta-delta
delta-star



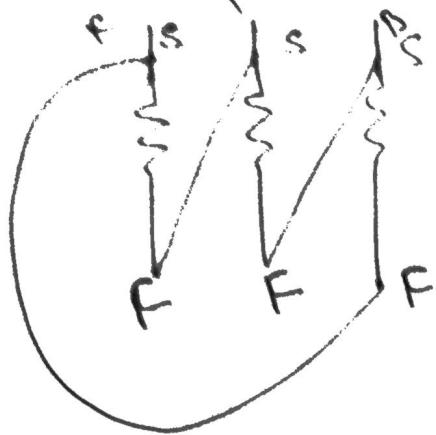

* CORE TYPE Transformer :-

In core type transformer the magnetic circuit consist of two sections namely two vertical section called limbs and two horizontal sections called yokes. The half of each winding is placed on each limb of the core. So that the flux leakage can be minimized. In the core type low V winding is always placed next to the core and the high voltage winding is placed around the low voltage winding. It is because it reduces the need of insulating material required.

→ Advantage - It is easier to dismantle for repair and maintenance.
Also it has efficient ~~so~~ natural cooling.

→ Disadvantage - It needs higher magnetizing current.

→ used in high voltage applications.

* Shell type transformer :-

A shell type transformer consists of one central limb as shown in the figure of shell-type transfo... In this both primary and secondary windings are placed on the central limb. The function of two outer limb is to create complete the path of low reluctance for magnetic flux.

In the shell type transformer each winding is divided on Subsections, where the low voltage winding and high voltage winding Subsections are alternatively placed on the central limb in form of a sandwich. for this reason the winding is called sandwich or disc winding.

Advantages - It gives better support against the electromagnetic forces between the current carrying conductors. Also the shell type transformer provides a shorter magnetic path than it requires smaller magnetizing current.
Disadvantage - It has poor natural cooling.

* used in low voltage applications such as low power C.R.Ls and electronic circuits
on the basis of Power:

Distribution transformer:

An electrical transformer which is employed in the power system near the load points for stepping down the high voltage to the safe rated utilization voltage is known as distribution transformer. Therefore, it is a stepdown transformer which reduces the supply voltage to the voltage level demanded by the consumer.

→ they have max^m eff. at 60% to 70% at the load.

Power transformer :-

An electrical transformer having very high MVA rating and is used to transmit high electric power at high voltage level through the power lines to the distribution centres is known as power transformer.

→ A power transformer is rated over 200 MVA with rating of 33 KV, 66 KV, 132 KV, 220 KV, 440 KV and so on. It is mainly used for increasing the low voltage level to a high voltage level for the transmission purpose. The power transformers are designed in such a way that they have maximum efficiency at or near the full load.

On the basis of voltage :-

Step-up transformer :-

A step-down transformer is one which has a primary voltage that is lower than the secondary voltage so if your building is wired with 208 V but you need 480 V to power a large machine, you will need a step-up transformer to boost the voltage 208 V to 480 V.

→ These examples are small industrial applications

→ Power companies use massive substation transformers called EHV transformers to step voltages up from power plants at 7200 V to extra-high voltage like 345,000 V for large-scale

power transmission over many miles.

Step-down transformer :-

→ A step-down transformer is one which has a primary voltage that is higher than the secondary voltage.

→ ~~The transformer~~, ~~the~~ transformer reduces the voltage from 11 KV to 220 & 440 for domestic and industrial use.

* Proof of Faraday's law :-

$$E_1 = -N_1 \frac{d}{dt} (\text{Flux linkage})$$

$$E_1 = -N_1 \omega B_m \sin(\omega t - \pi/2)$$

$$E_1(\text{max}) = N_1 \omega B_m \quad (\because \sin(\omega t - \pi/2) = 1)$$

$$E_1(\text{real}) = 2\pi f N_1 B_m, \quad E_1(\text{rms}) = 444 f N_1 B_m$$

$$\text{Similarly } E_2 = 444 f N_2 B_m$$

$$\boxed{\frac{E_2}{E_1} = \frac{N_2}{N_1}} = \frac{I_1}{I_2}$$

Three-phase transformer :-

A transformer which consists of three pairs of non-interfering windings placed in a three-section iron core, where each section contains a pair of a primary winding and a secondary winding, and is used to step-up or step-down the three-phase alternating voltage is known as three-phase transformer.

On the basis of connections :-

there are four types of transformer connections :-

1) Star-star connection

2) Star-delta connection

3) Delta-delta connection

4) Delta-delta connection.


Single-phase Transformer :-

A type of transformer which consists of only one pair of the transformer coils or winding, one primary winding and one secondary point winding and is used for transforming the single-phase alternating voltage to the desired value, is known as single-phase transformer.

Q. No. 10 is of 10% :-

Q) Draw a single line diagram showing transmission and distribution lines from generating station to end point.

Sol^m

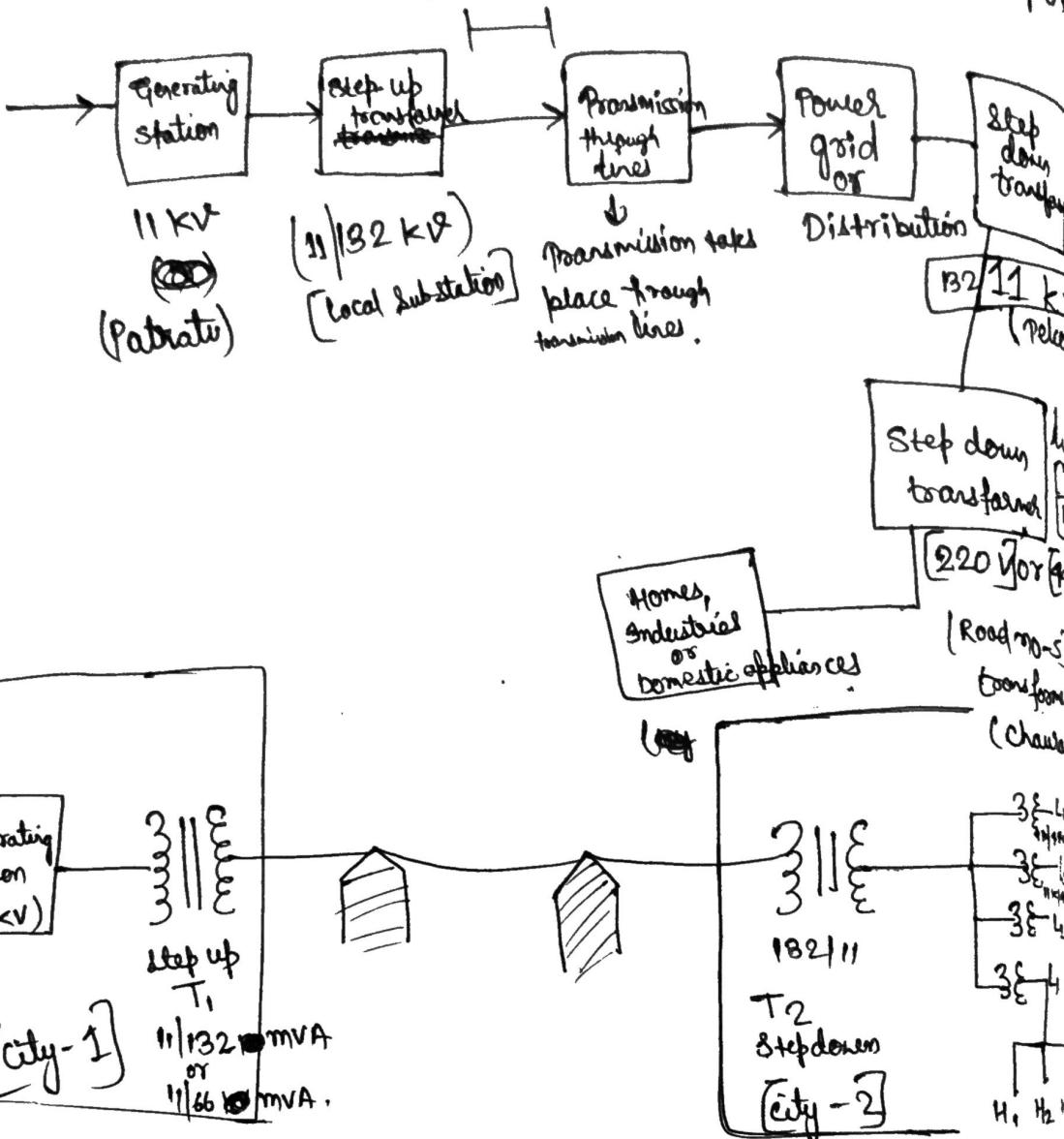

- Q) Why transformer rating is in KVA? Why not in KW?
- Q) Why core is laminated?
- Q) Which loss is greater Core or Copper & why?

Q) A 20 kVA single-phase transformer has 400 turns on primary and 4000 turns on secondary. The primary winding is connected to 230 V AC supply. Determine i) Secondary voltage at no load
ii) Primary & secondary currents at full load.

$$\text{SOL} \quad i) \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{4000}{400} \Rightarrow V_2 = \frac{V_1 \times N_2}{N_1} = \frac{230 \times 4000}{400} = 146.666 \text{ Volts.}$$

$$ii) I_{\text{Primary}} = \frac{P_{\text{Secondary}}}{2.2 \times 11000} = \frac{50}{2.2} = 22.7 \text{ A.}$$

$$P_{\text{Secondary}} = \frac{50 \times 50 \text{ KVA}}{146.66} = \frac{50 \times 1000}{146.66} = 341.06 \text{ A.}$$

Q) A single phase 4-kVA transformer has 400 primary turns & 1000 secondary turns, the net cross-sectional area of the core 60 cm². When the primary winding is connected to 500 V, 50 Hz supply calculate. i) the max. value of flux density in the core. ii) the voltage induced in the secondary winding and iii) the secondary full load current.

$$\text{SOL} \quad i) \phi = \frac{500}{\sqrt{2} \times \pi \times 50 \times 400 \times} = \frac{500}{88799.2} = 0.00568$$

$$\text{flux density} = \frac{0.00563}{60 \times 10^{-1}} = \frac{56.3}{60} =$$

$$ii) V_2 = \frac{N_2}{N_1} \times V_1 = \frac{1000}{400} \times 500 = 50 \times 25 = 1250.$$

$$\Rightarrow \frac{I_{\text{primary}}}{I_{\text{secondary}}} = \frac{4000}{1250} = 3.2 \text{ Amperes.}$$

Q) why transformer rating is in KVA not in KW?

Soln core losses are dependent on the input voltage
copper losses are dependent on the current running through the winding.

Hence total losses depend on voltage in joining to current but not upon power factor, thus the rating of the transformer is done in KVA not in KW.

Q) why core is laminated?

Soln The iron core of a transformer is laminated to reduce eddy current losses. Eddy currents are the small currents that result from the changing magnetic field created by the alternating current in the first coil. They need to be minimised so they won't disturb the flow of electricity from the primary coil to the secondary coil.

Q) Which loss is greater core loss or copper loss and why?

Soln A transformer has mainly two types of losses.

1) core losses

2) copper losses.

→ core loss : It is also referred as iron loss, consist of hysteresis loss and eddy current loss.

→ These two losses are constant when the transformer is


charged. That means the amount of these losses does not depend upon the condition of secondary load of the transformer. In all loading condition, these are fixed.

Copper loss is ^{also} referred as I^2R loss entirely depends upon load current (I). Hence copper loss are also known as variable loss.

→ Copper losses are due to the iron loss occurs due to variation of flux density in the transformer core and copper loss occurs due to I^2R in the transformer winding. The transformer is a static piece of equipment and there are no moving parts in it. Therefore the mechanical losses in the transformer are almost nil.

Q) Draw Y and Δ and Define what is line voltage & phase voltage?

Soln

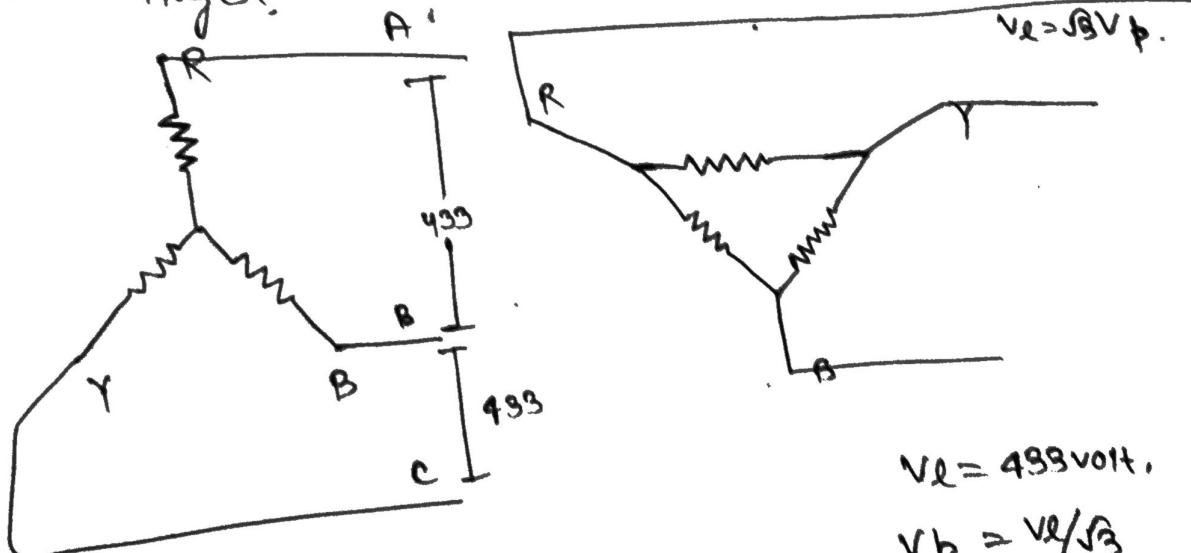

$$3 \text{ kVA} \quad P.v = 250 \text{ V} \quad H.V = 220 \text{ V} \Rightarrow I = 13.63 \text{ A}$$

$$\text{L.V} = 110 \text{ V} \Rightarrow I = 27.27 \text{ A.}$$

$$V_L = 433 \text{ volt.}$$

$$V_P = V_L / \sqrt{3}$$

$$V_P = 250 \text{ volt}$$


$$25 \text{ kVA} \quad \left\{ \begin{array}{l} H.V = 11000 \quad I = 2.27 \text{ A.} \\ L.V = 433 \quad I = 57.73 \text{ A.} \end{array} \right.$$

Q) Which core side winding area is more H.V or L.V side? 2a.

Soln

Q) Why transformer works on AC? & What will happen if transformer works on DC supply?

*

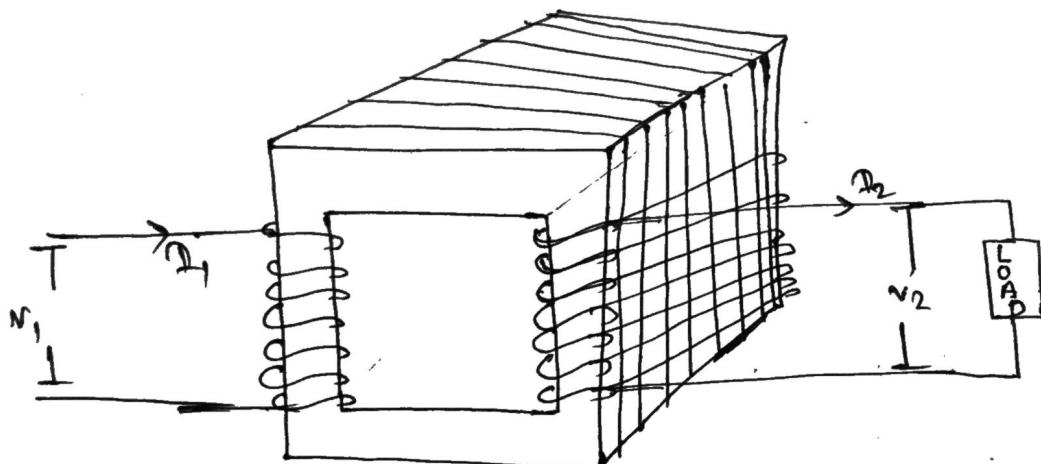

Soln

When an alternating voltage V_1 is applied to the primary, an alternating flux ϕ is setup in the core. This flux links both the windings and induces emf in them.

$$E = -N \frac{d\phi}{dt}$$

$$E = 4.44 f N \phi_{max}$$

Q) What is an ideal transformer?



Soln

① No漏磁

③ No power loss

② No Copper or Core loss

④ Efficiency 100%

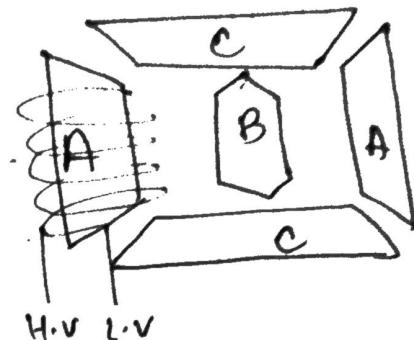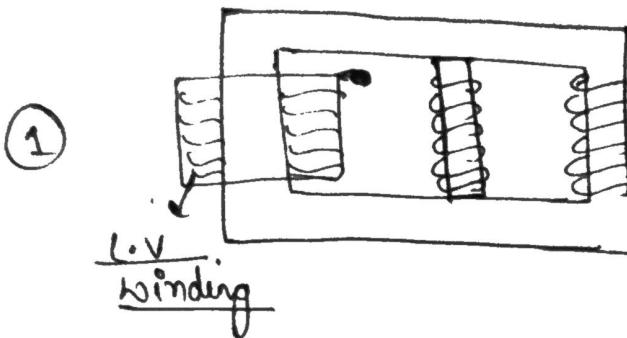

→ core thickness is between 1.8mm to 40.

Stacking factor

→ It is the ratio of effective cross-sectional area to the physical-cross sectional area is known as the stacking factor. These two are different because of the way cores are constructed.

Topic to read

→ Phasor diagram in case of ideal & no load transformer.

Homework :-


$$\phi = \Phi_m \sin \omega t$$

$$E_1 = -N_1 \frac{d\phi}{dt} = E_{1m} \sin(\omega t - \pi/2)$$

Similarly :-

$$E_2 = E_{2m} \sin(\omega t - \pi/2).$$
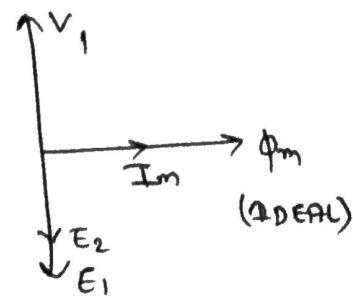
$$V_1 \rightarrow I_m \rightarrow \phi \rightarrow E_1$$




Practically (No Load)


$$I_D = I_M + I_W$$

I_W - Mag components | Reaction | wattless comp.

I_M - core loss components | Active | wattful comp.

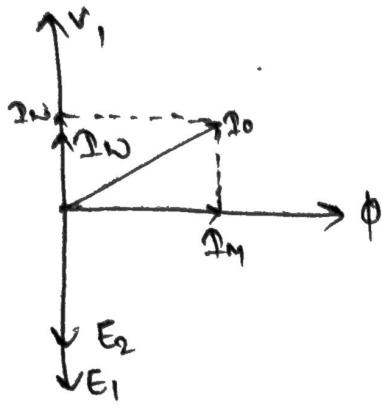

when load is connected :-

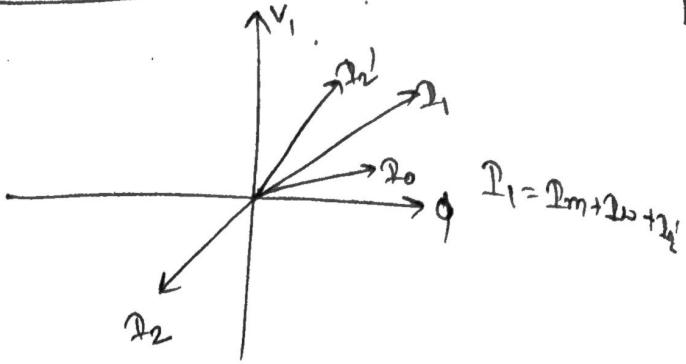


Soln low voltage winding can be primary. High voltage winding carries a lower current, hence the resistance of winding is more.


As the resistance of winding is inversely proportional to the area of cross section, the area of high voltage winding is less compared to low voltage winding.

Soln A constant DC source connected to the primary side of transformer will have zero emf. The constant current creates zero induced emf.

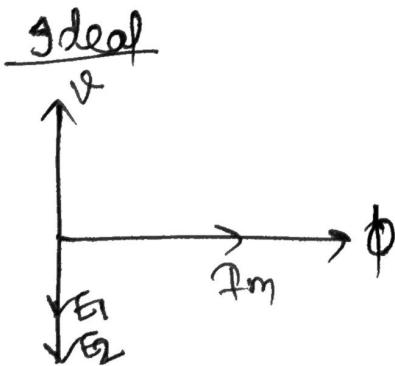* As a result primary side of transformer will behave short-ckt & heavy current will flow through primary which will in turn burn the winding.



No load (Practical)

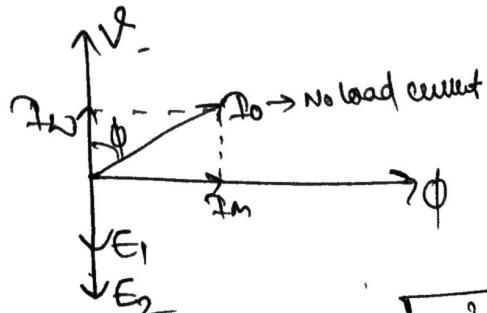

$$I_{\omega} = I_0 \cos \phi$$

$$I_m = I_0 \sin \phi$$

$$I_0 = \sqrt{I_{\omega}^2 + I_m^2}$$

Q) Why Φ is the reference?

Q) Principle of ideal transformer.

- ~~Q)~~
- 1) Primary & secondary windings of ideal transformer have negligible resistance.
 - 2) The core has infinite permeability so negligible current is required to flow the flux.
 - 3) Entire flux is confined in two windings \rightarrow means there is no leakage.
 - 4) There is no losses & efficiency is 100%.

Practical

-
-
-
-
-
-
-
- It is impossible to construct ideal transformer

Ideal

- Primary & secondary windings have some resistance.
- Efficiency is approx 93-98%.
- The core has finite permeability.
- Voltage regulation is never zero.
- There is some flux leakage.
- All constructed transformer are practical.


~~Q~~ ^{Home} A single phase transformer has 1000 turns on the primary & 200 turns on the secondary. The no-load current is 3-amps at P.f = 0.2 lag. Calculate the primary current and power factor when secondary current is 280 amperes at a p.f of 0.8 lagging.

~~Q~~ A 1000/200 volt transformer takes 0.3 amps at power factor of 0.2 on open ckt. Find the magnetizing and iron loss component of no load primary current.

Sol ~~V_p = 1000 volt.~~ ~~P_{no load} = 1000 × 0.3 = 300 watt.~~

$$I_W = \frac{P_0}{V_p} \cos \phi = 0.3 \times 0.2 = 0.06$$
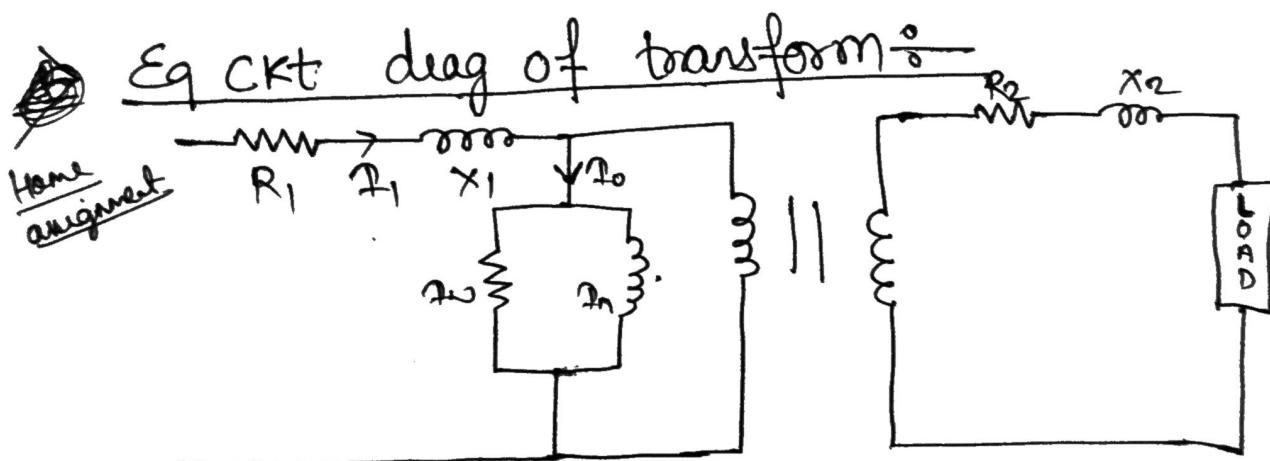
$$I_M = \frac{P_0}{V_p} \sin \phi = 0.3 \times 0.98 = 0.294$$



- Q) What is construction & working principle of transformer?
- Q) What is ideal cond'n of transformer?
- Q) What is difference b/w Ideal & practical transf.?
- Q) What are the parameters of eqⁿ ckt of transformer?
- Q) What is efficiency?
- Q) What is all day efficiency?
- Q) What is voltage regulation?

~~Q)~~ Explain phasor diagram? (Ideal case, no load case, load).

- there are resistive, capacitive, inductive.
- Q) Why polarity test is required and what will happen when we connect with wrong polarity.

Testing of a transformer

- 1) Ratio test
- 2) High voltage winding resistance test. [with the help of Wheatstone bridge]
- 3) Low voltage winding 11. [Kelvin double bridge]
- 4) Insulation resistance test. [Meger test] (Mohm)
- 5) Open ckt test. or [no-load test or iron loss test]
- 6) Short ckt test or [copper loss or load loss test].
- 7) Back to Back test
- 8) Polarity test.
- 9) DVDF test (Double voltage double freq test). Withstand test for 1 minute.
- 10) Swin burn test.
- 11) Impulse test
- 12) SCOTT connection test.

$\frac{V_2}{V_1}$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$I_P = \frac{N_2}{N_1} \times I_2 = \frac{240}{196} \times 28\phi = 56 A$$

$$\cos \phi_2 = 0.8, \quad \cos \phi_0 = 0.2, \quad \sin \phi_2 = 0.6.$$

$$\sin \phi_0 = 0.98$$

$$I_1 \cos \phi_1 = I_2 \cos \phi_2 + I_0 \cos \phi_0 = (56 \times 0.8) + (3 \times 0.2)$$

$$= 45.4 A.$$

$$I_1 \sin \phi_1 = I_2 \sin \phi_2 + I_0 \sin \phi_0 = (56 \times 0.6) + 3 \times 0.98$$


$$= 36.54 A.$$

$$I_1 = \sqrt{(45.4)^2 + (36.54)^2} = 58.3 A.$$


$$I_M = I_0 \sin \phi_0 = 3 \times 0.6 = 1.8 A.$$

$$\tan \phi_1 = \frac{36.54}{45.4} = 0.805, \quad \Rightarrow \phi_1 = 38^\circ.$$

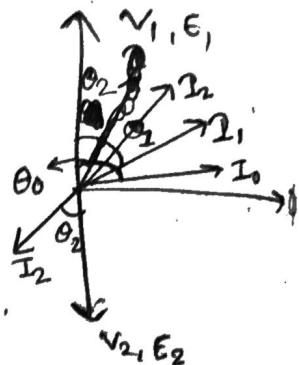P.f; $\cos \phi_1 = \cos 38^\circ = 0.78$ lagging.



Eq ckt diagram of transformer :-

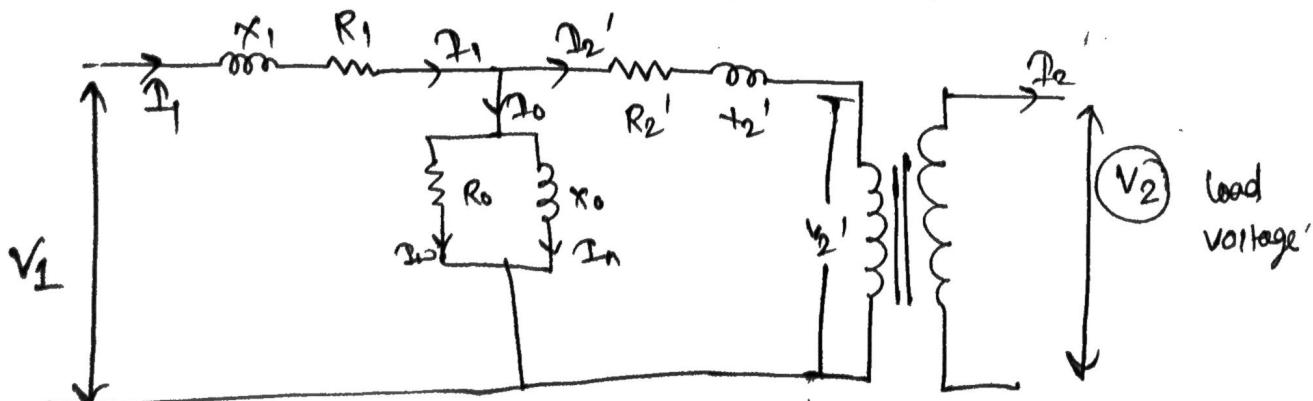


Equivalent ext reffed to primary - (T-circuit)

$$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2$$

$$X_2' = X_2 \left(\frac{N_1}{N_2} \right)^2$$

$$V_2' = V_2 \cdot \frac{N_1}{N_2}$$

Eq ckt referred to secondary

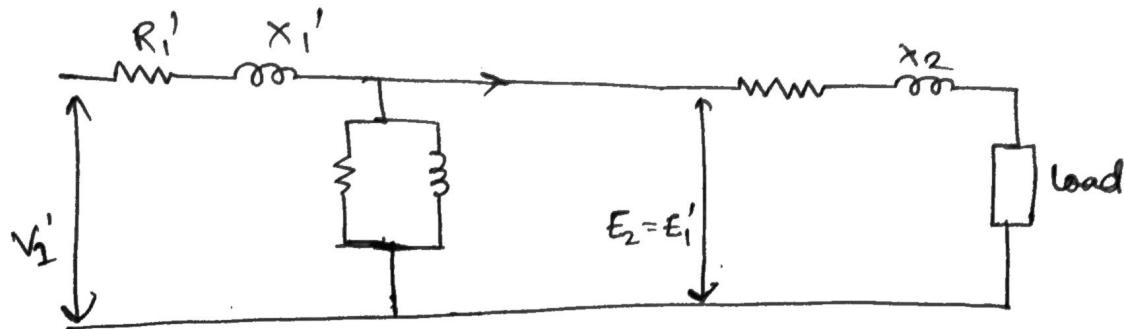

$$V_1' = V_1 \left(\frac{N_2}{N_1} \right)$$

$$R_1' = R_1 \left(\frac{N_2}{N_1} \right)^2$$

$$X_1' = X_1 \left(\frac{N_2}{N_1} \right)^2$$

$$R_0' = R_0 \left(\frac{N_2}{N_1} \right)^2$$


$$X_m' = X_m \left(\frac{N_2}{N_1} \right)^2$$

$$S_2' = S_1 \left(\frac{N_1}{N_2} \right)$$

$$S_0' = S_0 \left(\frac{N_1}{N_2} \right)$$

→ these ckt's are ~~co~~relatively complex / complicated so we need to approximate them

approximate them

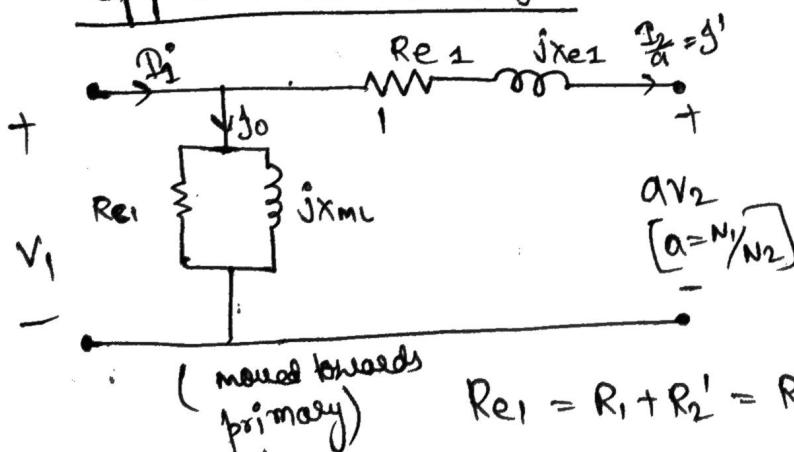

$$\alpha V_2 \quad [\alpha = \frac{N_1}{N_2}]$$


$$Re_1 = R_1 + R_2' = R_1 + R_2 \left(\frac{N_1}{N_2} \right)^2$$

• No load V_0 is ignored

• No load cu loss is ignored


• Core loss is over-estimated.
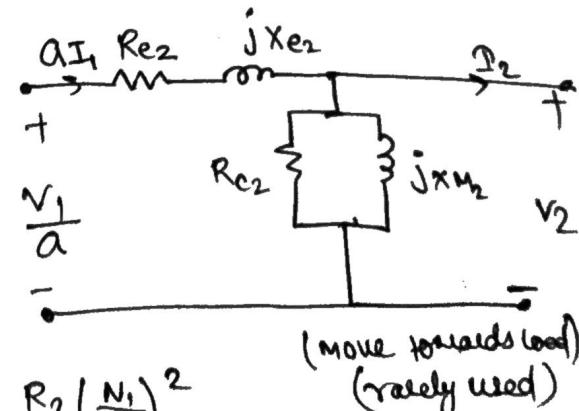
$$X_{e1} = X_1 + X_2' = X_1 + X_2 \left(\frac{N_1}{N_2} \right)^2$$



(move towards load)
(rarely used)

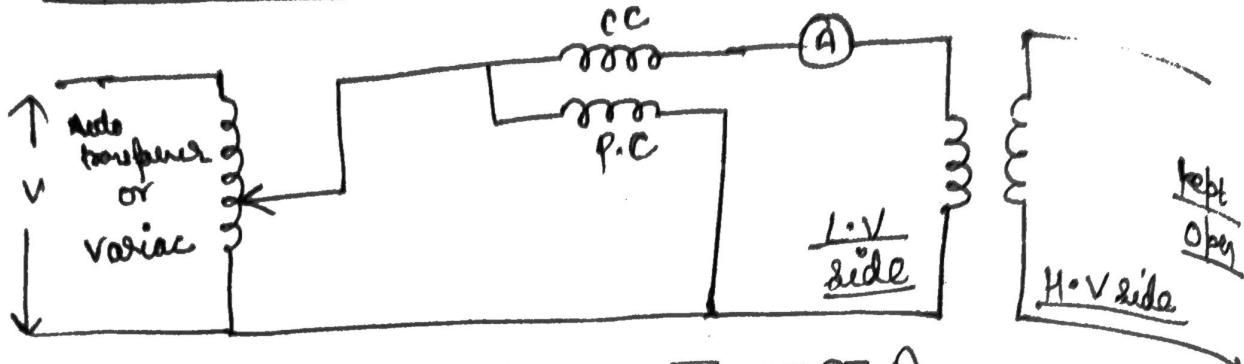Open ckt test [no load test or COTAN TEST (last test)].



3 KVA

$$\begin{aligned} L.V \rightarrow 110 &\rightarrow 27.27 \text{ A.} \\ H.V - 220 &\rightarrow 13.63 \text{ A} \end{aligned}$$

5 KVA

$$\begin{aligned} 220/110 &\rightarrow 45.44 \text{ A} \\ &\rightarrow 22.72 \text{ A} \end{aligned}$$

100 KVA


$$\begin{aligned} [11000/440] \quad I_{H.V} &= 9.09 \text{ A} \\ I_{L.V} &= 227 \text{ A.} \end{aligned}$$

5 MVA

$$\begin{aligned} [11000/440] \quad I_{H.V} &= 454.54 \text{ A} \\ I_{L.V} &= 11363.63 \text{ Amperes} \end{aligned}$$

→ the aim of this test is to determine the iron losses of the transformer. This test is performed at normal supply voltage & frequency. The primary winding ($L.V.$) is supplied with a normal voltage at normal frequency ^{preferable}. The other winding ($H.V.$) is kept open. From loss of voltmeter of low range are connected in the primary. No load current will be very small so small ammeter & load current will be approximately 3-4% of rated current.


Short ckt test :

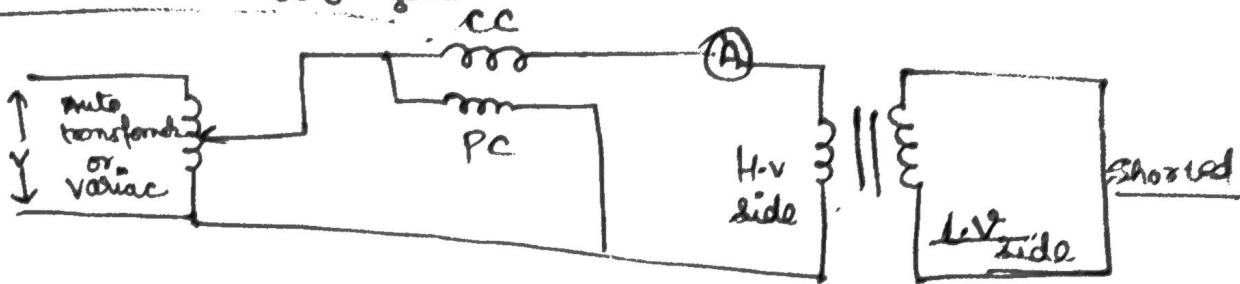

→ In the test primary Winding (H.V) is supplied the rated current or full load current with reduced voltage at normal frequency. This reduced is called impedance voltage. This impedance voltage is 3-8% of the rated voltage.


Homework solution:-

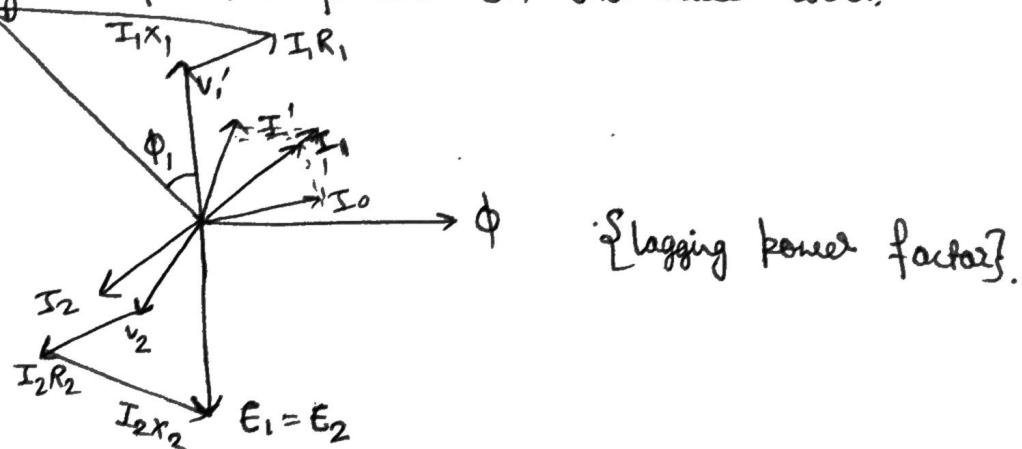① Phasor diagram of transformer on inductive load.



{lagging power factor}.

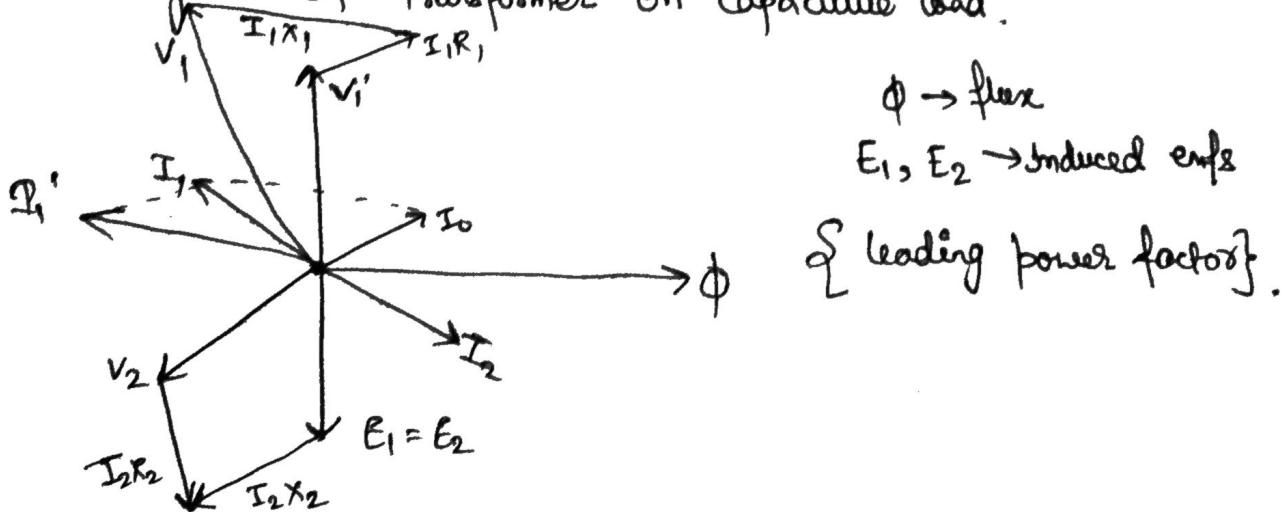
② Phasor diagram of Transformer on capacitive load.




$\phi \rightarrow$ flex
 $E_1, E_2 \rightarrow$ induced emfs

{leading power factor}.

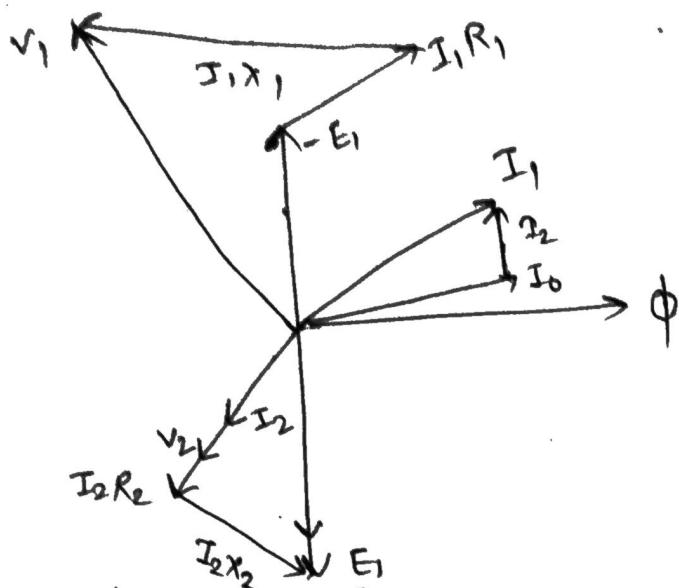(iii) Phasor diagram of transformer on Resistive load.



Polarity test:

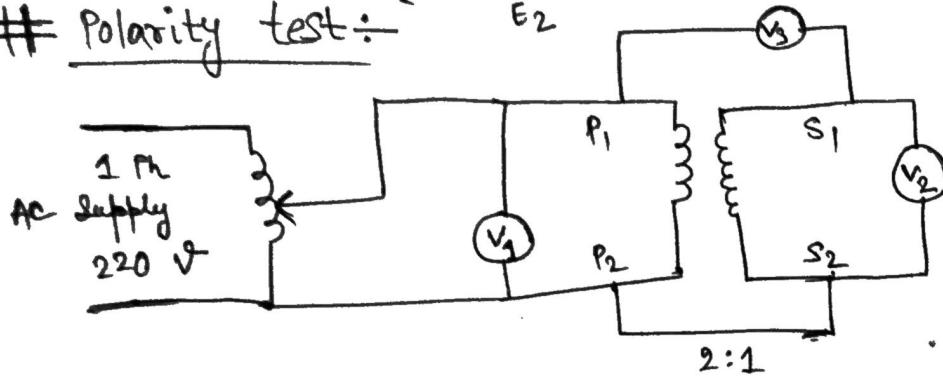

- We should know when we connect a transformer to AC supply that a particular instant one terminal of the primary, w.r.t to other terminal is positive or at higher potential.
- The purpose of polarity test to ensure that all single phase device (Switch, fuse, circuit breaker, MCB) etc certainly connected with lines.
- For parallel operation of two or more than two transformer ^{or load capacity} so that to increase the power delivered by transformer.


→ P_1 + S_1 are of the same polarity.

for similar polarity $\Rightarrow V_1 = 100 \quad V_2 = 50 \quad V_3 = (100 - 50) = 50 \text{ V}$.

→ for opposite polarity :

$$V_1 = 100 \text{ V}, \quad V_2 = 50 \text{ V}, \quad V_3 = 100 + 50 = 150 \text{ V}.$$

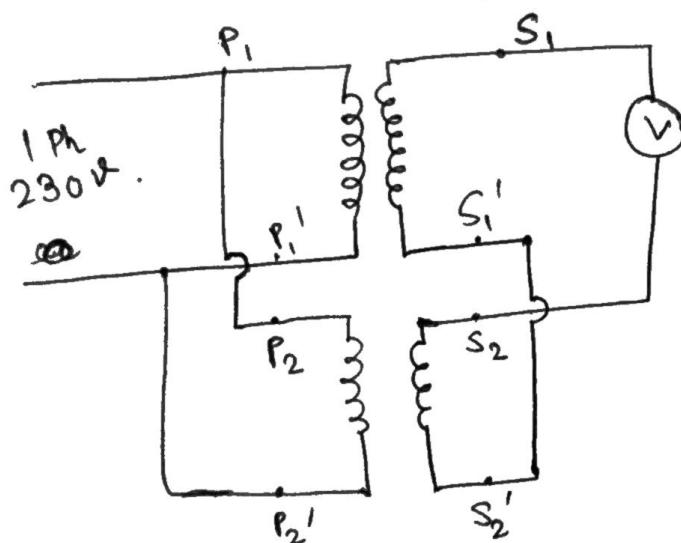→ we conclude that if V_3 is less than the applied voltage the terminal S_1 should be marked true whereas the voltmeter reads more than applied voltage it should be marked negative.



The two transformers to be connected in parallel should be connected that their primary & secondary have the same polarity. This can be done by conducting a polarity test.

- 1) Switch on the supply.
- 2) Note the reading in the voltmeter connected on the secondary side. It may be either 0 or twice the secondary terminal voltage.
- 3) If the voltmeter reads 0 the correct polarity has been connected.
- 4) If the voltmeter reads double then its Secondary opposite polarity has been connected, then terminal S_1 should be connected to S_2' .